

# Circuit Theory

Asst. Prof. Görkem SERBES

Introduction

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<http://yarb1s1.yildiz.edu.tr/gserbes>

# Course Details

- Course Code : BLM1612
- Course Name: Circuit Theory  
(Devre Teorisi)
- Instructor : Görkem SERBES

# Assessment

| Method          | Quantity | (%) |
|-----------------|----------|-----|
| Problem Solving | 5        | 5   |
| Laboratory      | 5+1      | 20  |
| Midterm Exam(s) | 2        | 40  |
| Final Exam      | 1        | 35  |

# Course Outline

## 1. Introduction.

Lumped circuit elements, Levels of abstraction, What are the circuits?, Course objectives.

## 2. Basic Concepts.

Units, Charge, Current, Voltage, Power, Conservation of Energy, Circuit Elements, Networks vs. Circuits, Ohm's Law, .

## 3. Voltage and Current Laws.

Circuit Terminology, Kirchhoff's Current Law, Kirchhoff's Voltage Law, The Single-Loop Circuit, Conservation of Energy, The Single-Node-Pair Circuit, Series Circuits, Parallel Circuits, Voltage Division, Current Division.

## 4. Nodal and Mesh Analysis.

Nodal (or "Node-Voltage") Analysis, Nodal Analysis with Supernodes, Mesh (Current) Analysis, Mesh Analysis with Supermeshes, Equivalent Practical Sources.

## 5. Linearity & Superposition.

Linearity, Superposition, Superposition: Voltage Sources, Superposition: Current Sources, Practical Voltage Sources, Practical Current Sources.

## 6. Thevenin & Norton Equivalents.

Thevenin Equivalent, Power from a Practical Source, Maximum Power Transfer .

## 7. The Operational Amplifier.

The Operational Amplifier, Inverting Amplifier, Noninverting Amplifier, Voltage Follower, Summing Amplifier, Difference Amplifier, Op-Amp Cascades, Op-Amp Parameters, Common Mode Rejection, Saturation, An instrumentation amplifier.

# Course Outline

## 8. Capacitors and Inductors.

Capacitance, Capacitor Current & Voltage, Capacitor Characteristics, Inductance, Inductor Current & Voltage, Inductor Characteristics, Inductor Energy Storage, DC Capacitor Circuits, DC Inductor Circuits.

## 9. Basic RL and RC Circuits.

The Source-Free RL Circuit, The Source-Free RC Circuit, Unit-Step Definition, Driven RL Circuit, Driven RC Circuit.

## 10. RLC Circuits.

Parallel RLC Circuit, Series RLC Circuit, RLC Solution: Over-damped, RLC Solution: Critically Damped, RLC Solution: Under-damped, The Complete Response Of The RLC Circuit.

## 11. AC Analysis.

Complex numbers, phasors, impedance, admittance, Sinusoidal steady-state; Ohm's Law, KVL, KCL for AC circuits, Sinusoidal steady-state: Thevenin, superposition, examples.

## 12. The Frequency Response.

Frequency response: transfer function, logarithms, Bode plots.

Frequency response: resonance, passive & active filter design

## 13. Laplace Transform.

Laplace: introduction to transforms, inverse transform.

Laplace: theorems, solving differential equations

## 14. s-Domain analysis

s-Domain analysis: transfer functions, poles, zeroes.

s-Domain analysis: nodal, mesh, additional techniques

# COURSE OBJECTIVE

- Students will be able to:
  - Analyze wide range of pure resistive DC circuits using the different techniques covered throughout the course.
  - Gains hands-on experience in DC circuit problem solving tricks and shortcuts.
  - Utilize the Thevenin theorem as a core tool in circuit analysis.
  - Analyze RL, RC, and RLC circuits with the proper tools.
  - Carry power consumption calculation for different components in a DC circuit.
  - Design, simulate, and implement Basic DC circuits.


# Main course book

## Engineering Circuit Analysis

by William Hayt, Jack  
Kemmerly, Steven  
Durbin.

Published by McGraw-Hill.

Isbn: 0073529575

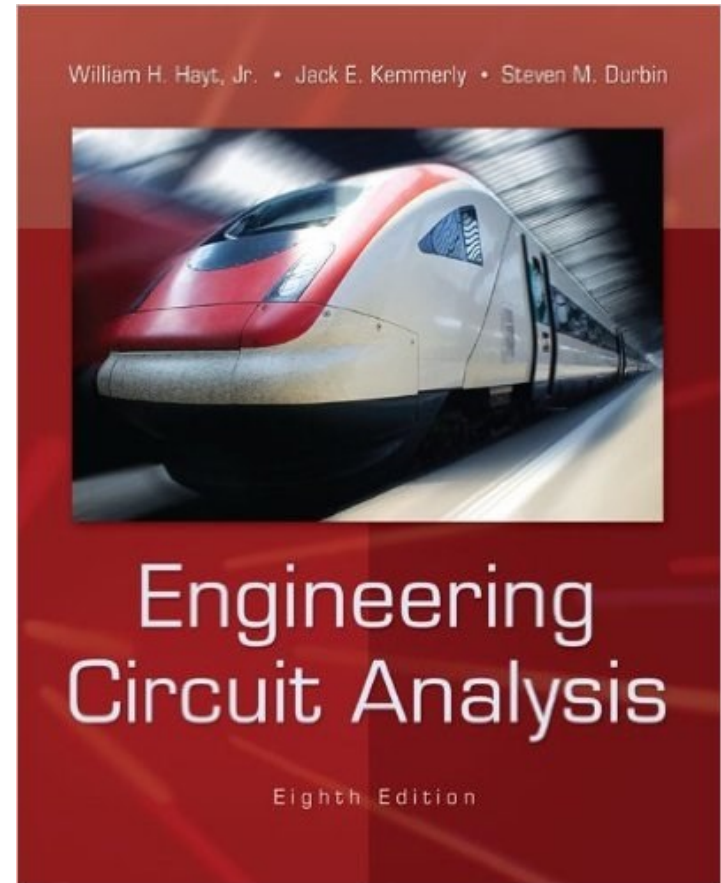

# Rules of the Conduct

- No eating /drinking in class
  - *except water*
- Cell phones must be kept outside of class or switched-off during class
  - *If your cell-phone rings during class or you use it in any way, you will be asked to leave and counted as unexcused absent.*
- No web surfing and/or unrelated use of computers,
  - *when computers are used in class or lab.*



# Rules of the Conduct

- You are responsible for checking the class web page often for announcements.
- Academic dishonesty and cheating will not be tolerated and will be dealt with according to university rules and regulations
  - *Presenting any work, or a portion thereof, that does not belong to you is considered academic dishonesty.*
- University rules and regulations:
  - <http://www.ogi.yildiz.edu.tr/category.php?id=17>
  - [https://www.yok.gov.tr/content/view/544/230/lang,tr\\_TR/](https://www.yok.gov.tr/content/view/544/230/lang,tr_TR/)

# Attendance Policy


- The requirement for attendance is **70%**.
  - *Hospital reports are not accepted to fulfill the requirement for attendance.*
  - *The students, who fail to fulfill the attendance requirement, will be excluded from the final exams and the grade of **F0** will be given.*

# Abstraction

- We have electromagnetic phenomena and this data can be expressed by using Maxwell's equations. (Scientific part)
- Electrical engineers create a new abstraction layer on top of Maxwell's equations called the **lumped circuit abstraction**.
- By using this lumped circuit abstraction electrical and computer systems can be designed.
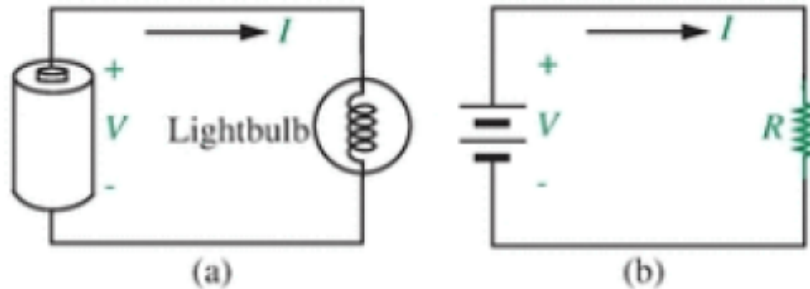
# Lumped circuit element


- A lumped circuit element is often used as an abstract representation or a model of a piece of material with complicated behaviour.



a) A simple light bulb circuit b) The lumped circuit representation


- $R$  is a lumped element abstraction for the bulb.
- A lumped element is described by its  $v-i$  (voltage - current) relation.

# Levels of abstraction


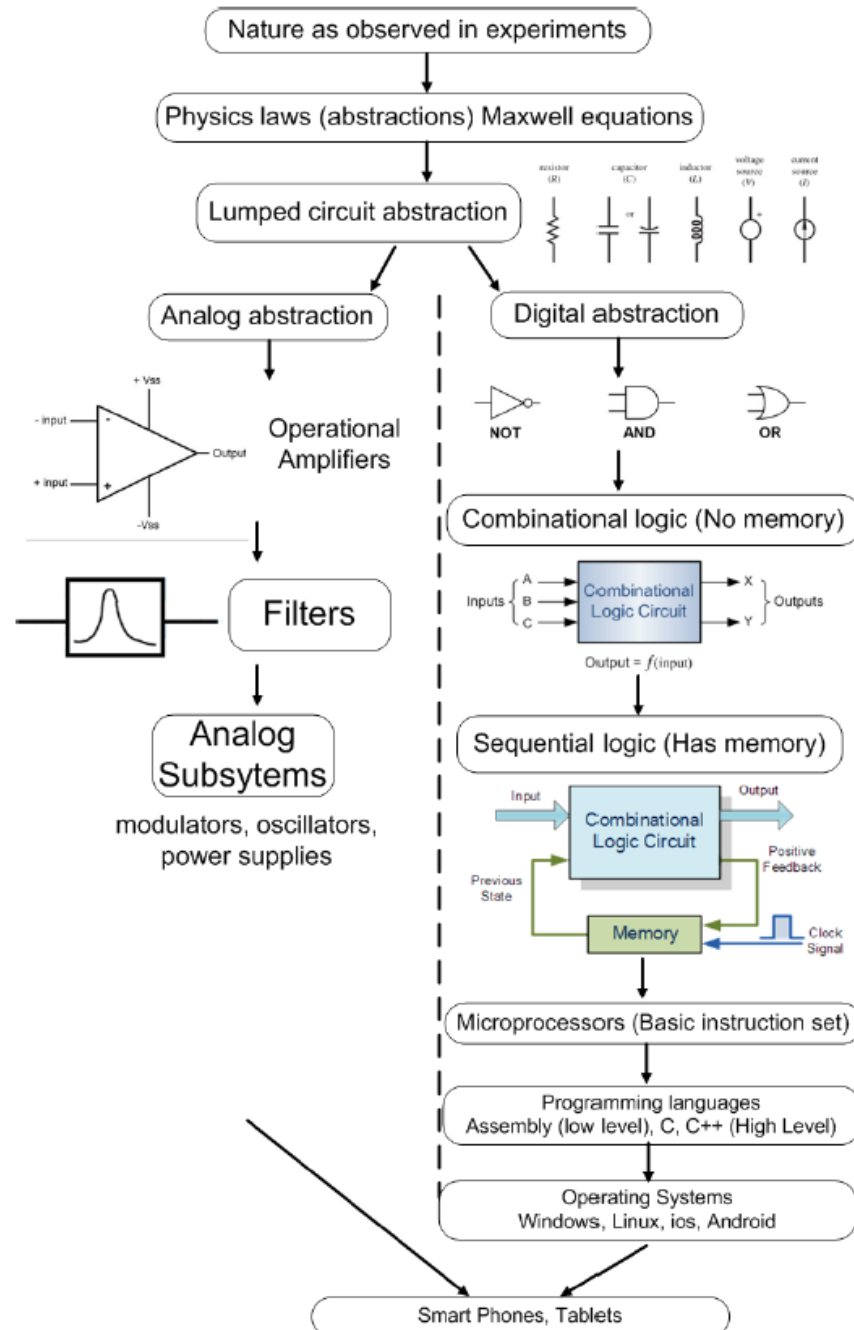

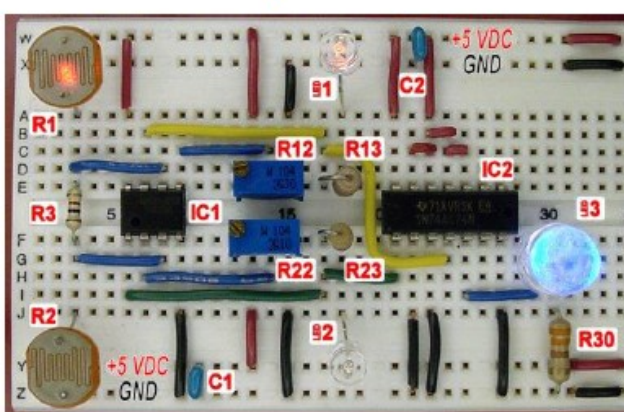
# What are the circuits?


- A *circuit* consists of electrical or electronic components interconnected with metal wires.
- Every electrical or electronic device is a circuit.



Breadboard

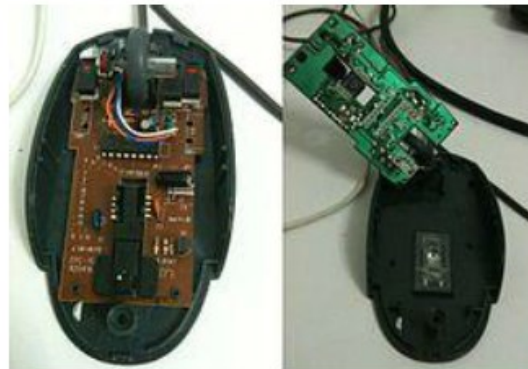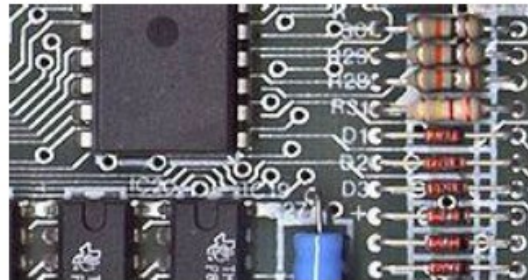

Printed Circuit Boards (PCBs)

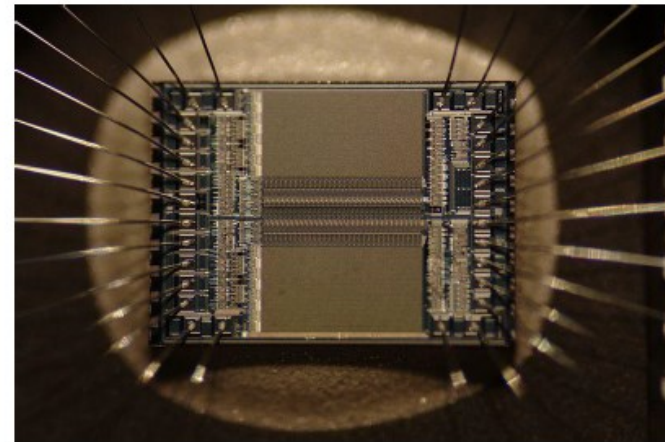

Integrated Circuits (ICS)




# Course objectives

- (1) to understand the electromagnetic concepts of charge, voltage, current, power, and energy

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

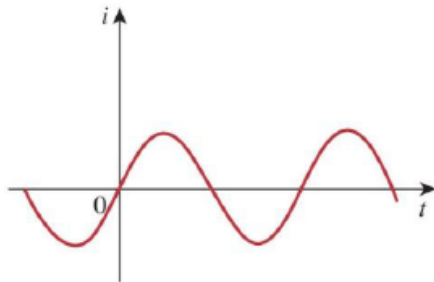

(b)

|   | Alternating Current (AC)                             | Direct Current (DC)   |
|---|--|---|
| <b>Amount of energy that can be carried</b> | Safe to transfer over longer city distances          | Voltage of DC cannot travel very far until it begins to lose energy |
| <b>Frequency</b>                            | The frequency of alternating current is 50Hz or 60Hz | The frequency of direct current is zero                             |
| <b>Direction</b>                            | It reverses its direction while flowing in a circuit | It flows in one direction in the circuit                            |
| <b>Obtained from</b>                        | A.C Generator  | Cell or Battery   |
| <b>Magnitude</b>                            | Magnitude varying with time                          | Constant magnitude  |

a) DC, b) AC


# Course objectives

- (2) to understand the function of **linear circuit elements** (e.g. resistors, inductors, capacitors, voltage sources, current sources, operational amplifiers)
  - a linear circuit is an electric circuit in which **circuit parameters** (Resistance, inductance, capacitance) are **constant**.
  - a **nonlinear circuit** is an electric circuit whose parameters are **changing** with respect to current and voltage (diodes, transistors)



# Course objectives

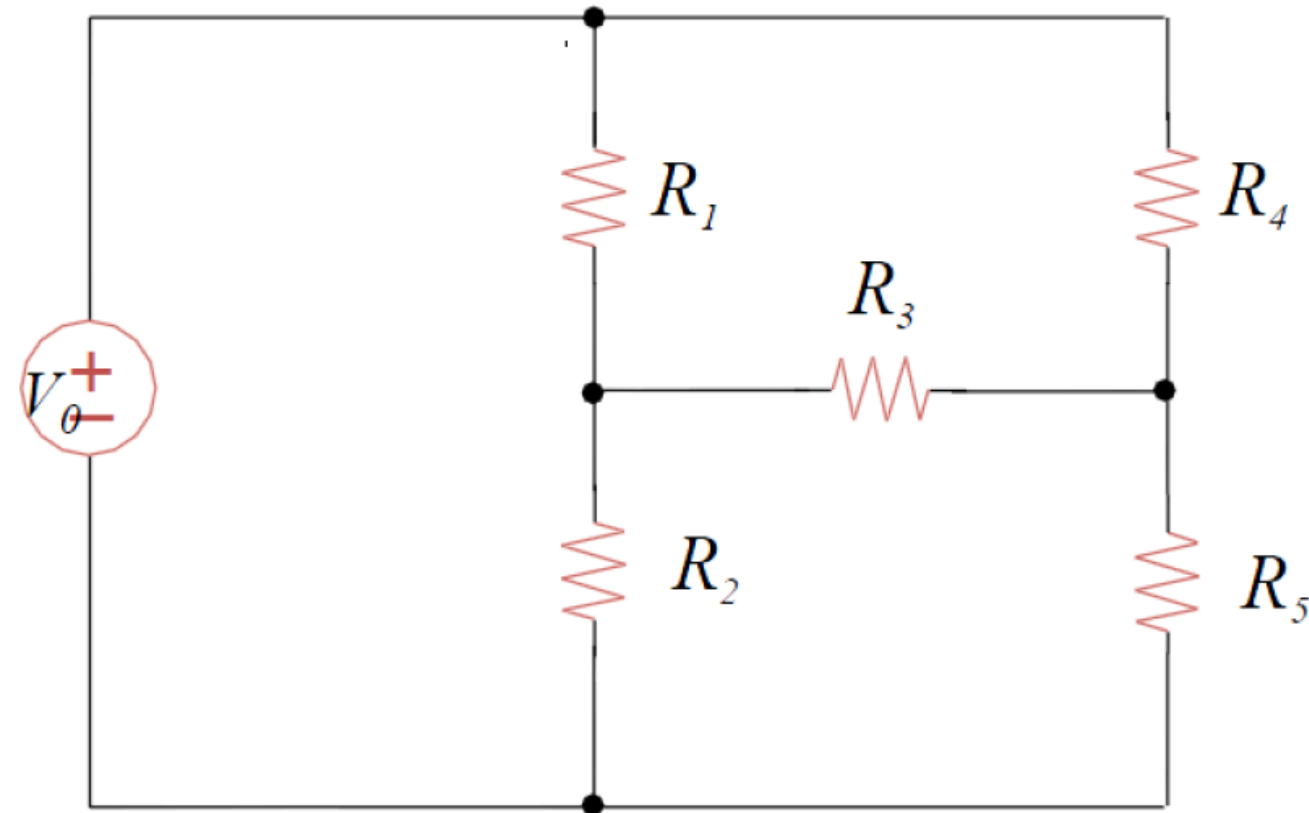- (3) to understand and apply circuit theory (e.g. Ohm's Law, Kirchhoff's Voltage & Current Laws)




-A simple circuit can be analysed with KVL and KCL but lots of equations must be solved.

- So, easier methods are needed.

# Course objectives

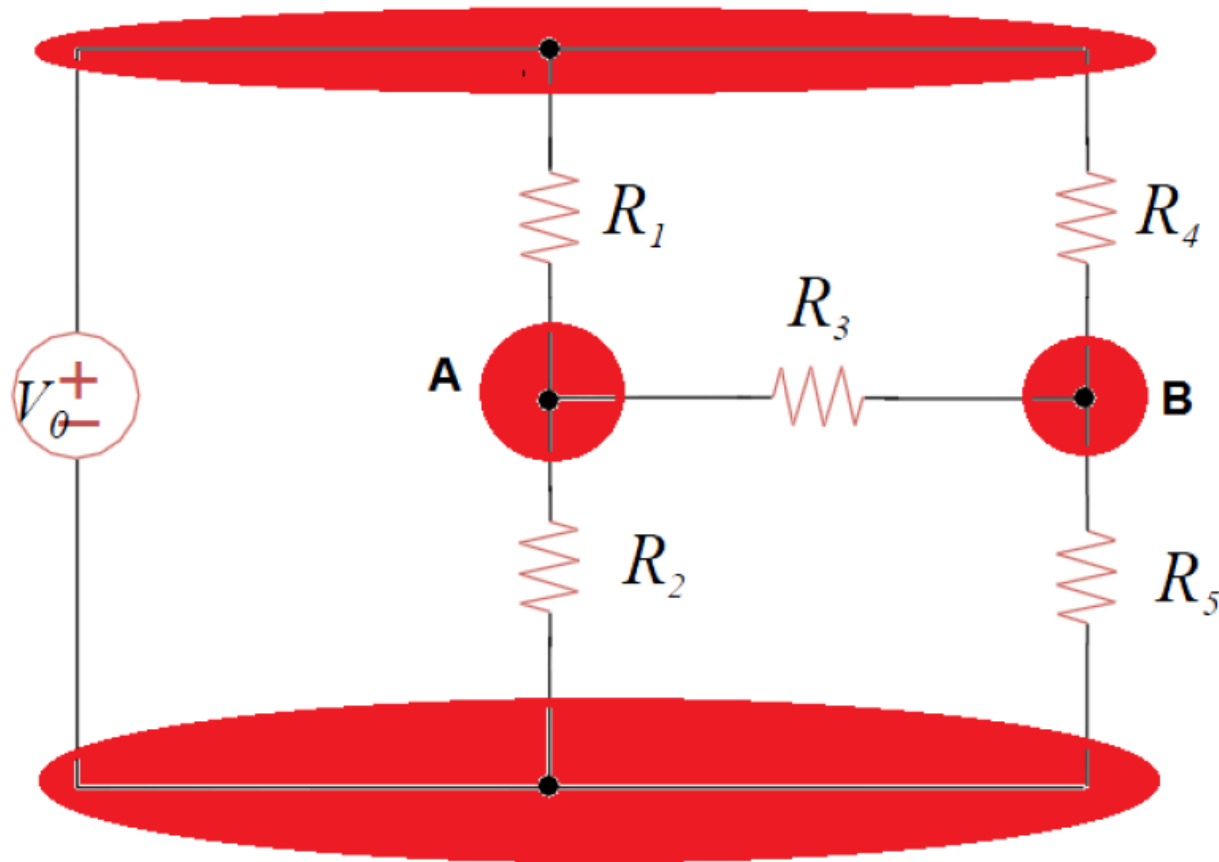
- (4) to apply linear analysis techniques (nodal, mesh, superposition, source transformation, Thevenin & Norton equivalents) to compute Direct Current circuit responses




- In nodal analysis, same circuit can be solved by using two node equations (A, B)

# Course objectives

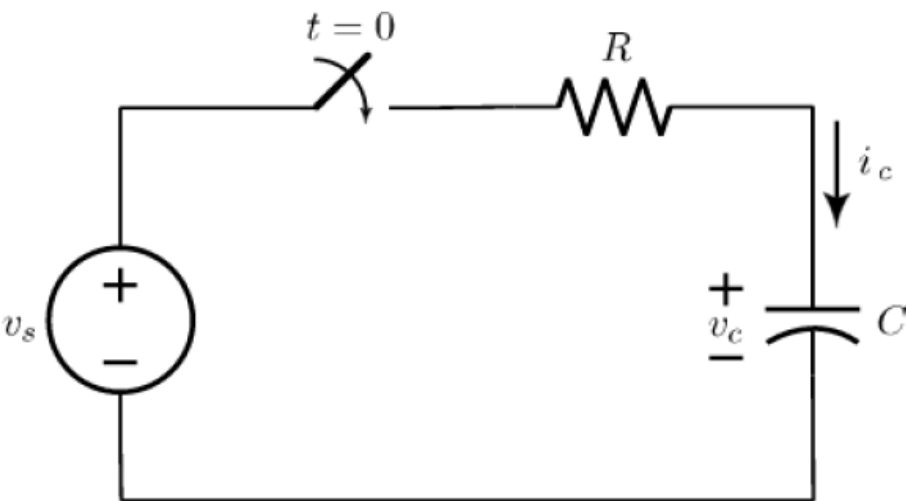- (5) to compute the transient and steady-state responses of first- and second-order linear circuits



A first order RC circuit

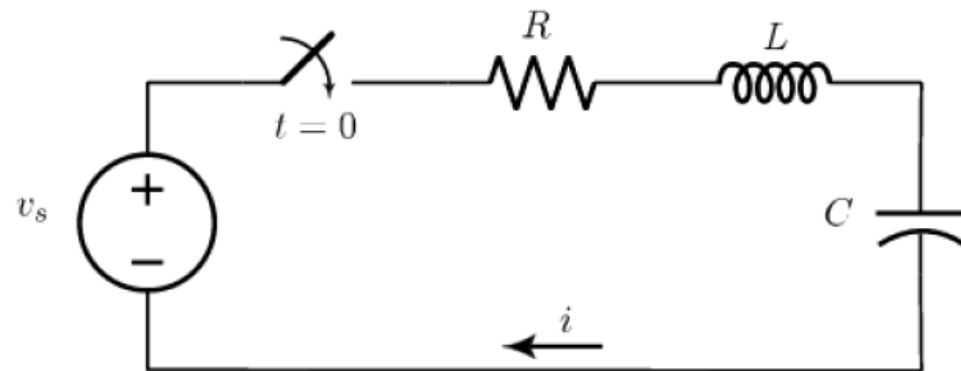


A second order RLC circuit

# Course objectives

- (6) to determine the linear steady-state responses of Alternating Current circuits using phasors

Time Domain

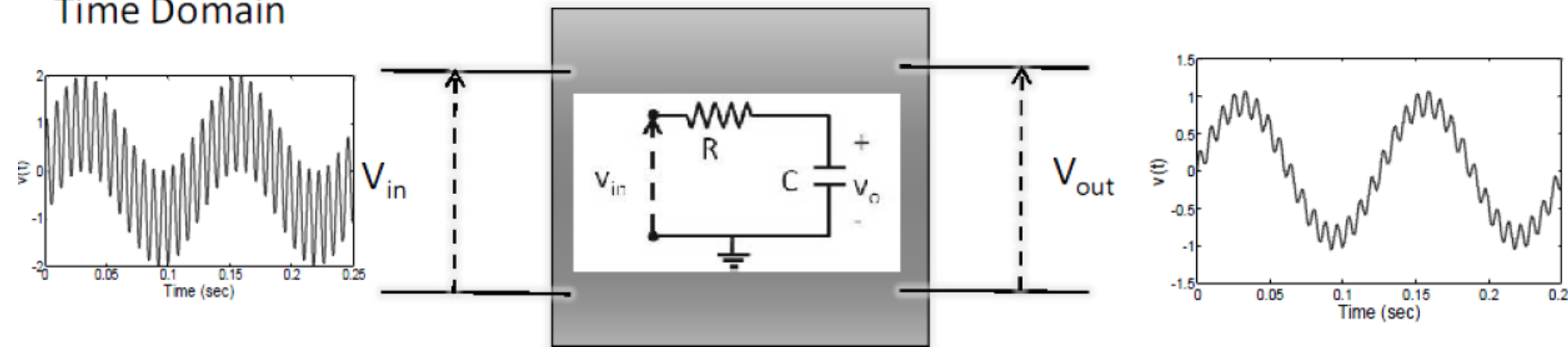

$$v(t) = V_m \cos(\omega t + \theta)$$


Amplitude:  $V_m$

Period:  $T$  sec

$$\text{Frequency (Hz): } f = \frac{1}{T}$$

$$\text{Frequency (rad/sec): } \omega = 2\pi f$$
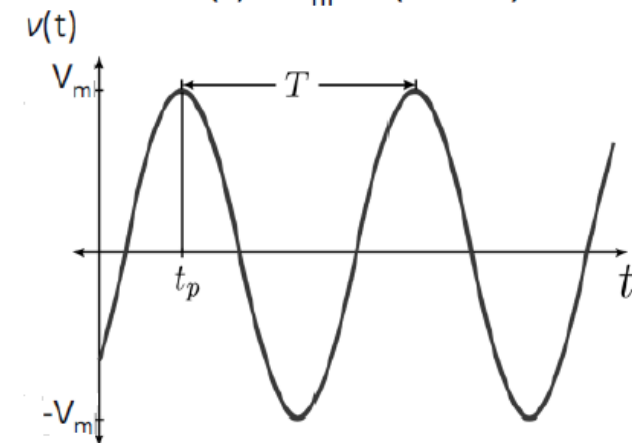
$$\text{Phase Angle: } \theta = -2\pi \frac{t_p}{T}$$




# Linear vs. Nonlinear

- Linear problems are inherently more easily solved than their nonlinear counterparts.
- For this reason, we often seek reasonably accurate **linear approximations** (or *models*) to physical situations.
- The linear models are more easily manipulated and understood which makes **analysis** and **design** a more straightforward process.

# Analysis and Design

- ***Analysis*** is the process through which we determine the scope of a problem, obtain the information required to understand it, and compute the parameters of interest.
- ***Design*** is the process by which we synthesize something **new** as part of the solution to a problem.
- A crucial part of design is analysis of potential solutions!

# Problem-Solving Strategies

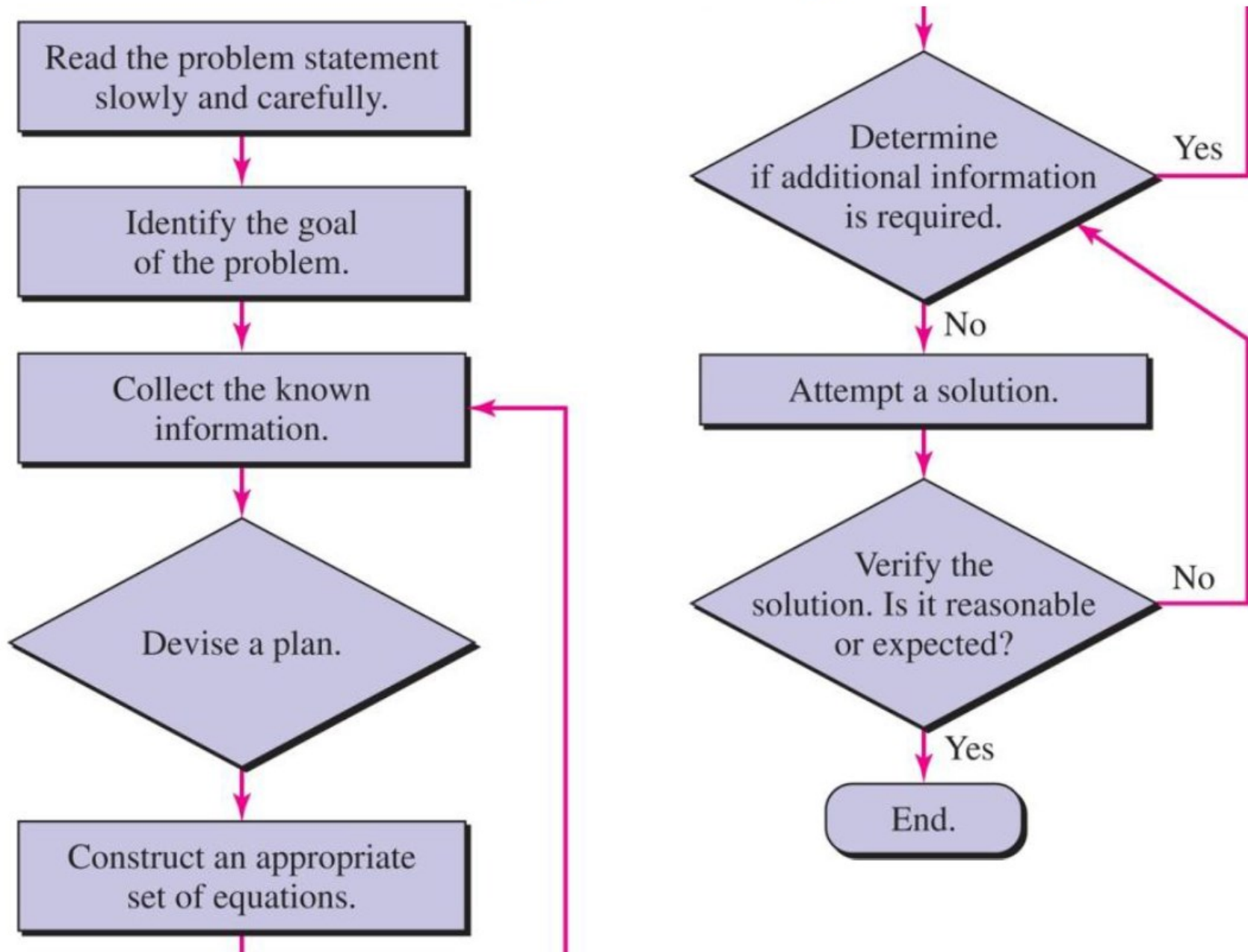



# Solving Linear Equations

Assume that we must solve a system of equations:

$$\begin{array}{rclclcl} 7v_1 & - & 3v_2 & - & 4v_3 & = & -11 \\ -3v_1 & + & 6v_2 & - & 2v_3 & = & 3 \\ -4v_1 & - & 2v_2 & + & 11v_3 & = & 25 \end{array}$$

- could solve these equations by systematic elimination of variables
- quicker way: using matrices, let a computer/calculator perform the required operations

***MatLab*** can be used.



# Matrix solution to linear equations

Step 1: Identify the coefficients and variables...

$$G = \begin{bmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{bmatrix} \quad B = \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix} \quad V = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

coefficients                      variables

Step 2: Write the equations in matrix form...

$$G \cdot V = B \quad \begin{bmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix}$$

Step 3: Perform the required operations...

$$\begin{aligned} G \cdot V &= B \\ G^{-1} \cdot G \cdot V &= G^{-1} \cdot B \\ V &= G^{-1} \cdot B \end{aligned}$$

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{bmatrix}^{-1} \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}$$

$$v_1 = 1 \text{ V}, v_2 = 2 \text{ V}, v_3 = 3 \text{ V}$$

# Matrix inversion

$$V = G^{-1} \cdot B \quad \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{bmatrix}^{-1} \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}$$

A matrix multiplied by its inverse equals the **identity matrix** (ones on the main diagonal, zeroes off the diagonal).

$$G^{-1} \cdot G = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

We will use Matlab to solve for  $G^{-1}$ .

$$G^{-1} = \begin{bmatrix} .325 & .215 & .157 \\ .215 & .319 & .136 \\ .157 & .136 & .173 \end{bmatrix}$$

# MatLab Procedure

```
>> G = [7 -3 -4;-3 6 -2;-4 -2 11]
```

```
G =
```

```
    7    -3    -4  
   -3     6    -2  
   -4    -2    11
```

```
>> G^-1
```

```
ans =
```

```
    0.3246    0.2147    0.1571  
    0.2147    0.3194    0.1361  
    0.1571    0.1361    0.1728
```

# MatLab Procedure

```
>> B = [-11;3;25]
```

```
B =
```

```
-11
```

```
3
```

```
25
```

```
>> V = G^-1 * B
```

```
V =
```

```
1.0000
```

```
2.0000
```

```
3.0000
```

# Examples


Rewrite the following systems of equations in matrix format and solve:

$$\begin{aligned} \text{(b)} \quad & 300I_1 - 250I_2 - 400I_3 = 10 \\ & -250I_1 + 375I_2 - 125I_3 = 0 \\ & -400I_1 - 125I_2 + 725I_3 = 7.5 \end{aligned}$$


```
>> G = [           ; ...  
           ; ...  
           ];  
>> B = [ ; ; ];  
>> I = G^-1 * B  
  
I = -0.0734  
     -0.0626  
     -0.0409
```
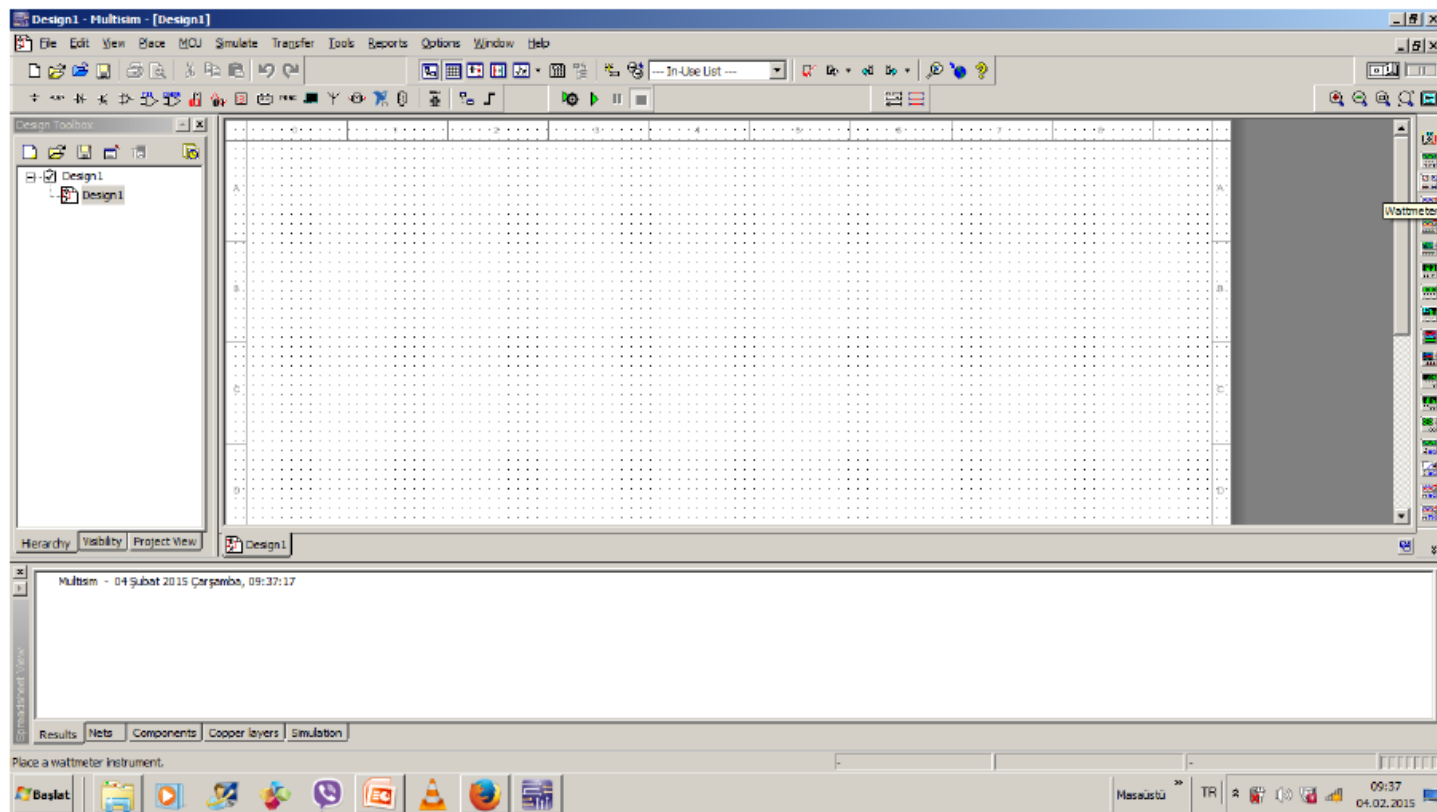
# Multisim

- Multisim is a powerful **schematic capture** and **simulation** environment that engineers and students can use to simulate electronic circuits and prototype Printed Circuit Boards (PCBs).



# Multisim Examples

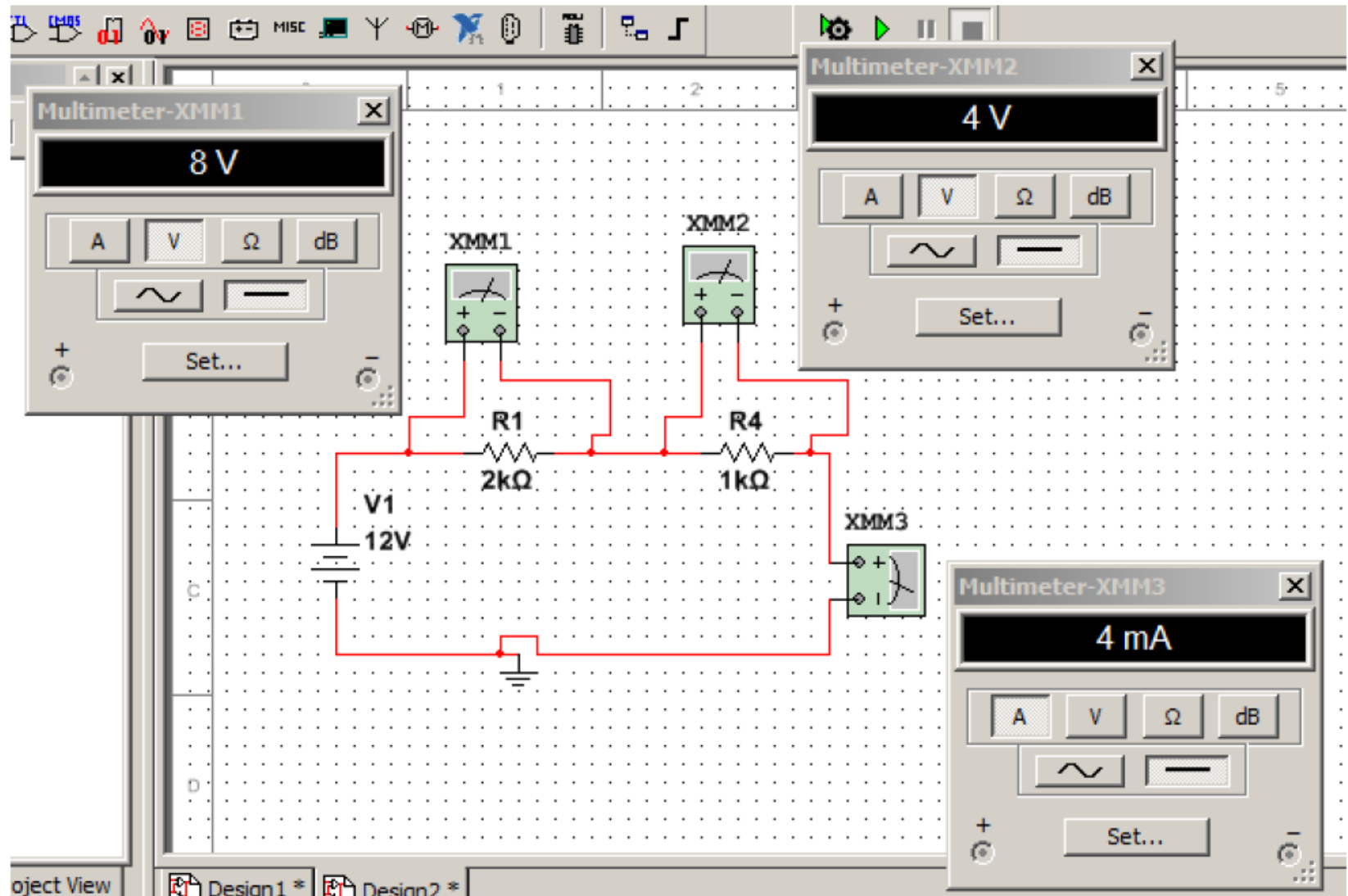

# Multisim Examples

